

Contents

Foreword	v
Preface	vii

ELECTRIC CIRCUITS

Chapter 1

BASIC CIRCUIT CONCEPTS (D.C. CIRCUITS) 3

• Introduction • Elements of an electric circuit
• Independent and dependent sources • Passive elements
• Bilateral and unilateral elements • The electric current
• The ampere • The electric potential • Potential difference • Volt • E.M.F. of a source • Ohm's law
• Limitations of Ohm's law • Power • Energy
• Resistance • Resistances in series • Resistances in parallel
• Current in a parallel branch • Self inductance • Energy stored in an inductor • Capacitance • Energy stored in a capacitor • Kirchhoff's laws • Cramer's rule • Procedure for solving electric circuits using Kirchhoff's laws • Linear networks • Source transformation • Source shifting • Star-delta transformation.

Chapter 2

MESH CURRENT AND NODE VOLTAGE ANALYSIS 56

• Introduction • A.C. fundamentals • Mesh current analysis
• Procedure for solving an electric circuit using mesh current analysis • Super mesh analysis • Node voltage analysis • Procedure for solving an electric circuit using node voltage analysis • Super nodal analysis
• Network containing dependent sources.

Chapter 3

NETWORK THEOREMS

105

• Introduction • Superposition theorem • Thevenin's theorem • Norton's theorem • Procedure for solving networks using Thevenin's theorem • Procedure for solving networks using Norton's theorem • Maximum power transfer theorem • Reciprocity theorem • Millman's theorem • Compensation theorem (Substitution theorem) • Tellegan's theorem.

Chapter 4

RESONANCE

169

• Introduction • Series resonance • The quality factor • Variation of reactances with frequency • Selectivity and bandwidth • Effect of R on frequency response curve • Effect of L/C on frequency response curve • Expressions for f_1 and f_2 • Relation between f_r , f_1 and f_2 • Resonance by varying circuit elements L and C • Variation of V_R , V_L and V_C w.r.t. frequency • Frequency deviation • Expressions for $f_{C_{\max}}$ and $f_{L_{\max}}$ • Parallel resonance • Practical parallel resonant circuit • Parallel resonant circuit considering the capacitance to have resistance • A general parallel resonant circuit • Variation of susceptances with frequency • Q factor of a parallel resonant circuit • Comparison between series and parallel resonance.

Chapter 5

NETWORK TOPOLOGY

214

• Introduction • Definitions • Graph of a network • Oriented graph • Tree and co-tree • Network variables • All incidence matrix • Reduced incidence matrix • Kirchhoff's current law and matrix A • Equilibrium equations with node to datum voltages as variables • Branch admittance matrix • The node admittance matrix • Number of possible trees of a graph • Cut-set • Fundamental cut-set • Cut-set schedule • Twig voltages and matrix Q • Kirchhoff's current law and matrix Q • Equilibrium equations with tree-branch voltages as variables • Tie-set and tie-set schedule • Kirchhoff's current law equations and matrix B • Branch voltages and matrix B • Equilibrium equations with loop currents as variables • The branch impedance matrix • E shift and I shift • Duality • Construction of dual networks • Construction of dual graphs.

Chapter 6

LOCUS DIAGRAMS

305

- Introduction • $R-X_L$ series circuit • $R-X_C$ series circuit
- $R-X_L-X_C$ series circuit • Locus diagrams of parallel circuits.

Chapter 7

COUPLED CIRCUITS

340

- Introduction • Mutual inductance • Coefficient of coupling • Mutual inductance between two coils which are connected on the same magnetic material • Dot convention • Coupled coils in series aiding and series opposition • Coupled coils in parallel aiding and parallel opposition.

Chapter 8

THREE PHASE BALANCED CIRCUITS

368

- Introduction • Advantages of three phase systems
- Generation of three phase voltages • Three phase connections • Measurement of power in a three phase circuit • Two wattmeter method.

Chapter 9

THREE PHASE UNBALANCED CIRCUITS

385

- Introduction • Phase sequence • Unbalanced delta connected load • Unbalanced star connected load
- Three phase, three wire unbalanced system • Star-delta conversion method • Maxwell's loop current analysis
- Displacement neutral method • Unbalanced 4 wire star connected system.

NETWORK ANALYSIS

Chapter 10

NON-SINUSOIDAL WAVEFORMS

431

- Introduction • Wave analysis • Wave symmetry • Effective value of a non-sinusoidally varying quantity • Power due to a non-sinusoidal wave • Circuit analysis when the waveforms are non-sinusoidal.

Chapter 11

INITIAL CONDITIONS

462

• Introduction • Initial conditions in elements • Procedure for finding the initial conditions • Final conditions in a network.

Chapter 12

LAPLACE TRANSFORMATION

507

• Introduction • The laplace transformation • Laplace transform of standard functions • Procedure to use laplace transformation • Partial fraction expansion • Heaviside's partial fraction expansion theorem
• First shifting theorem • Second shifting theorem
• Convolution theorem • Initial value theorem • Final value theorem • Laplace transform of unit impulse function
• Unit step function • Unit ramp function
• Laplace transform of periodic function • Step response (Dumahel's superposition integral) • Transformed networks
• Gate function.

Chapter 13

NETWORK FUNCTIONS

578

• Introduction • One port network • Two port network • Poles and zeros of network functions • Pole-zero plot • Physical significance of poles and zeros • Time domain response from pole-zero plot • Restrictions on poles and zeros locations.

Chapter 14

TWO PORT PARAMETERS

604

• Introduction • Short-circuit admittance parameters (y parameters) • Open circuit impedance parameters (z parameters) • Transmission parameters (T parameters)
• Inverse transmission parameters (T' parameters)
• Hybrid parameters (h parameters) • Inverse hybrid parameters (g parameters) • Relation between y parameters and other types of parameters • Relation between z parameters and other types of parameters • Relation between T parameters and other types of parameters
• Relation between h parameters and other types of parameters • Relation between T' and g parameters with other types of parameters • Cascade connection of two port networks: • Series connection of two ports • Parallel connection of two ports • Permissibility of interconnection of

two port networks • T section representation of a two port network • π section representation of a two port network.

Chapter 15

NETWORK SYNTHESIS

647

-
- Introduction • Positive real function (PRF) • Hurwitz polynomials • Synthesis of networks • Properties of L-C immittance functions • Synthesis of L-C immittance functions
 - First foster form • Second foster form
 - First cauer form • Second cauer form • Properties of R-C impedance functions and R-L admittance functions
 - Synthesis of R-C impedance of R-L admittance functions
 - Properties of R-L impedance functions and R-C admittance functions • Synthesis of R-L impedance functions and R-C admittance functions.

Answers to Numerical Problems

685

Index

733
